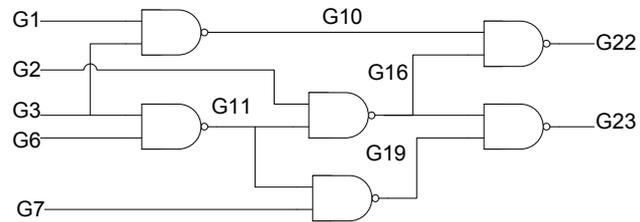


The S17 circuit



Faults according to the Stuck-at Fault model:

- F1: SA0 on G10
- F2: SA1 on G10
- F3: SA0 on G11
- F4: SA1 on G11
- F5: SA0 on G16
- F6: SA1 on G16
- F7: SA0 on G19
- F8: SA1 on G19

Optional assignment:

If you opt for this assignment, don't turn the page until you are done.
Generate test patterns for these faults (by hand).
After compaction, four test patterns is reasonable.

	<u>Test set</u>					
	G1	G2	G3	G6	G7	
TP1	0	1	1	1	0	F1(G22), F4(G22,G23), F5(G22,G23), F7(G23)
TP2	1	0	1	0	1	F2(G22), F3(G23), F8(G23)
TP3	0	1	1	0	0	F3(G22,G23), F6(G22,G23)

Optional assignment:

If you opt for this assignment, don't turn the page until you are done.

Construct a fault dictionary for the faults on the previous page and the test patterns from this page.

	<u>Fault dictionary</u>								
	F1	F2	F3	F4	F5	F6	F7	F8	
TP1	1	0	0	3	3	0	2	0	(*)
TP2	0	1	2	0	0	0	0	2	
TP3	0	0	3	0	0	3	0	0	


- 0: No fault on any output
- 1: Fault on output G22
- 2: Fault on output G23
- 3: Fault on both G22 and G23

(*) The test set cannot differentiate between fault F4 and fault F5.

Assignment:

Generate a test pattern to complement the test set from the previous page (TP1 to TP3), such that the test set can differentiate between the faults F4 and F5.

The S17 circuit

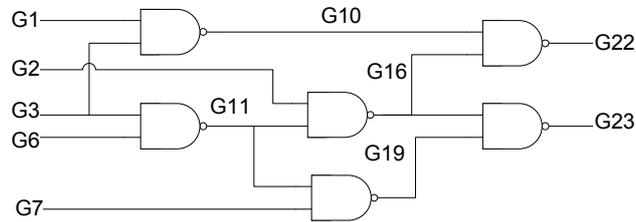

Faults according to the Stuck-at Fault model:

- F1: SA0 on G10
- F2: SA1 on G10
- F3: SA0 on G11
- F4: SA1 on G11
- F5: SA0 on G16
- F6: SA1 on G16
- F7: SA0 on G19
- F8: SA1 on G19

Assignment:

Using a single fault-assumption, categorize the faults according to the the different combinations of faulty/non-faulty signatures that can be read on the primary outputs.

When you are done, compare with your fault dictionary.

Also compare your result with the location of the faults.

How effective is analysis of the faulty/non-faulty signature on the outputs in localising the fault in this example?

G22	G23	
V	V	No faults
V	X	?
X	V	?
X	X	?